


CHARLES A. SCHULER

# Electronics

Principles and Applications

TENTH EDITION


Mc  
Graw  
Hill

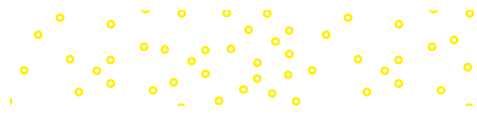

Tenth Edition


# Electronics


Principles & Applications

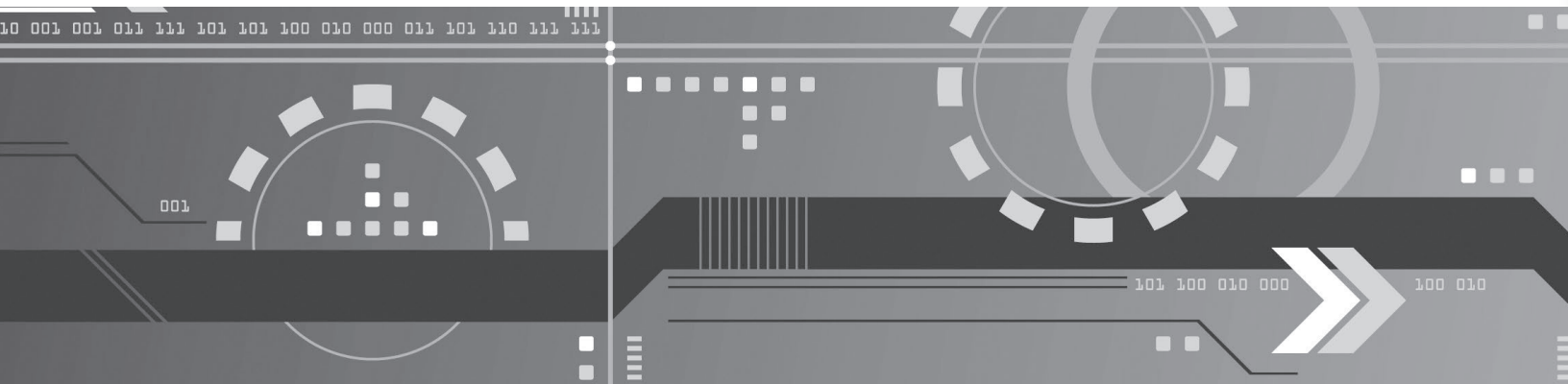

Charles A. Schuler

Mc  
Graw  
Hill

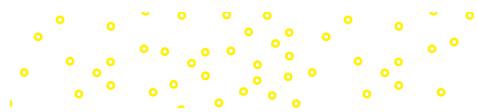

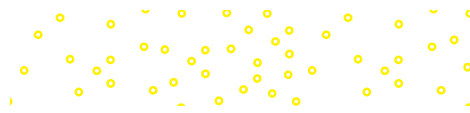

## ELECTRONICS

Published by McGraw Hill LLC, 1325 Avenue of the Americas, New York, NY 10019. Copyright ©2024 by McGraw Hill LLC. All rights reserved. Printed in the United States of America. No part of this publication may be reproduced or distributed in any form or by any means, or stored in a database or retrieval system, without the prior written consent of McGraw Hill LLC, including, but not limited to, in any network or other electronic storage or transmission, or broadcast for distance learning.

Some ancillaries, including electronic and print components, may not be available to customers outside the United States.

This book is printed on acid-free paper.

1 2 3 4 5 6 7 8 9 LKV 28 27 26 25 24 23


ISBN 978-1-266-22005-0

MHID 1-266-22005-4

Cover Image: *Image Source/Perry Mastrovito*

All credits appearing on page or at the end of the book are considered to be an extension of the copyright page.

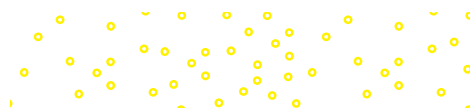The Internet addresses listed in the text were accurate at the time of publication. The inclusion of a website does not indicate an endorsement by the authors or McGraw Hill LLC, and McGraw Hill LLC does not guarantee the accuracy of the information presented at these sites.



# Contents

Preface . . . . .	v	<b>Chapter 5 Transistors</b>	<b>105</b>
About the Author . . . . .	vii	5-1 Amplification . . . . .	105
Walkthrough . . . . .	x	5-2 Transistors . . . . .	107
Acknowledgments . . . . .	xiv	5-3 Characteristic Curves . . . . .	113
Safety . . . . .	xv	5-4 Transistor Data . . . . .	117
<b>Chapter 1 Introduction</b>	<b>1</b>	5-5 Transistor Testing . . . . .	119
1-1 A Brief History . . . . .	1	5-6 Other Transistor Types . . . . .	122
1-2 Digital or Analog . . . . .	4	5-7 Power Transistors . . . . .	126
1-3 Analog Functions . . . . .	7	5-8 Transistors as Switches . . . . .	138
1-4 Circuits with Both DC and AC . . . . .	10	<b>Chapter 6 Introduction to Small-Signal Amplifiers</b>	<b>149</b>
1-5 Trends in Electronics . . . . .	14	6-1 Measuring Gain . . . . .	149
<b>Chapter 2 Semiconductors</b>	<b>21</b>	6-2 Common-Emitter Amplifier . . . . .	157
2-1 Conductors and Insulators . . . . .	21	6-3 Stabilizing the Amplifier . . . . .	165
2-2 Semiconductors . . . . .	24	6-4 Other Configurations . . . . .	171
2-3 N-Type Semiconductors . . . . .	26	6-5 Simulation and Models . . . . .	176
2-4 P-Type Semiconductors . . . . .	27	<b>Chapter 7 More about Small-Signal Amplifiers</b>	<b>184</b>
2-5 Majority and Minority Carriers . . . . .	29	7-1 Amplifier Coupling . . . . .	184
2-6 Other Materials . . . . .	30	7-2 Voltage Gain in Coupled Stages . . . . .	190
2-7 Band Gaps . . . . .	31	7-3 Field-Effect Transistor Amplifiers . . . . .	198
<b>Chapter 3 Diodes</b>	<b>34</b>	7-4 Negative Feedback . . . . .	205
3-1 The PN Junction . . . . .	34	7-5 Frequency Response . . . . .	212
3-2 Characteristic Curves of Diodes . . . . .	38	7-6 Positive Feedback . . . . .	217
3-3 Diode Lead Identification . . . . .	41	<b>Chapter 8 Large-Signal Amplifiers</b>	<b>225</b>
3-4 Diode Types and Applications . . . . .	44	8-1 Amplifier Class . . . . .	225
3-5 Photovoltaic Energy Sources . . . . .	56	8-2 Class A Power Amplifiers . . . . .	229
<b>Chapter 4 Power Supplies</b>	<b>65</b>	8-3 Class B Power Amplifiers . . . . .	233
4-1 The Power-Supply System . . . . .	65	8-4 Class AB Power Amplifiers . . . . .	238
4-2 Rectification . . . . .	66	8-5 Class C Power Amplifiers . . . . .	243
4-3 Full-Wave Rectification . . . . .	68	8-6 Switch-Mode Amplifiers . . . . .	248
4-4 Conversion of RMS Values to Average Values . . . . .	71	<b>Chapter 9 Operational Amplifiers</b>	<b>257</b>
4-5 Filters . . . . .	76	9-1 The Differential Amplifier . . . . .	257
4-6 Voltage Multipliers . . . . .	81	9-2 Differential Amplifier Analysis . . . . .	261
4-7 Ripple and Regulation . . . . .	86	9-3 Operational Amplifiers . . . . .	266
4-8 Zener Regulators . . . . .	88	9-4 Setting Op-Amp Gain . . . . .	271
4-9 Troubleshooting . . . . .	91	9-5 Frequency Effects in Op Amps . . . . .	277
4-10 Replacement Parts . . . . .	95	9-6 Op-Amp Applications . . . . .	280
		9-7 Comparators . . . . .	298

**Chapter 10 Troubleshooting 306**

10-1 Preliminary Checks . . . . . 306  
10-2 No Output . . . . . 314  
10-3 Reduced Output . . . . . 319  
10-4 Distortion and Noise . . . . . 324  
10-5 Intermittents . . . . . 328  
10-6 Operational Amplifiers . . . . . 331  
10-7 Automated Testing . . . . . 333  
10-8 Thermal Issues . . . . . 338  
10-9 Software Updates . . . . . 340

**Chapter 11 Oscillators 346**

11-1 Oscillator Characteristics . . . . . 346  
11-2 RC Circuits . . . . . 349  
11-3 LC Circuits . . . . . 357  
11-4 Crystal Circuits . . . . . 360  
11-5 Relaxation Oscillators . . . . . 364  
11-6 Undesired Oscillations . . . . . 368  
11-7 Oscillator Troubleshooting . . . . . 372  
11-8 Direct Digital Synthesis . . . . . 374  
11-9 DDS Troubleshooting . . . . . 376

**Chapter 12 Communications 384**

12-1 Modulation and Demodulation . . . . . 384  
12-2 Simple Receivers . . . . . 390  
12-3 Superheterodyne Receivers . . . . . 392  
12-4 Other Modulation Types . . . . . 396  
12-5 Wireless Data . . . . . 403  
12-6 Troubleshooting . . . . . 410

**Chapter 13 Integrated Circuits 420**

13-1 Introduction . . . . . 420  
13-2 Fabrication . . . . . 423  
13-3 The 555 Timer . . . . . 430  
13-4 Analog ICs . . . . . 436  
13-5 Mixed-Signal ICs . . . . . 437  
13-6 IC Communication Protocols . . . . . 450  
13-7 Troubleshooting . . . . . 451

**Chapter 14 Electronic Control Devices and Circuits 461**

14-1 Introduction . . . . . 461  
14-2 The Silicon-Controlled Rectifier . . . . . 463  
14-3 Full-Wave Devices . . . . . 469  
14-4 Feedback in Control Circuitry . . . . . 475  
14-5 Managing Energy . . . . . 483  
14-6 Troubleshooting Electronic Control Circuits . . . . . 487

**Chapter 15 Regulated Power Supplies 494**

15-1 Open-Loop Voltage Regulation . . . . . 494  
15-2 Closed-Loop Voltage Regulation . . . . . 500  
15-3 Current and Voltage Limiting . . . . . 506  
15-4 Switch-Mode Regulators . . . . . 514  
15-5 Power Factor Correction . . . . . 521  
15-6 Troubleshooting Regulated Power Supplies . . . . . 523


**Chapter 16 Digital Signal Processing 537**

16-1 Overview of DSP Systems . . . . . 537  
16-2 Moving-Average Filters . . . . . 542  
16-3 Fourier Theory . . . . . 546  
16-4 Digital Filter Design . . . . . 550  
16-5 Other DSP Applications . . . . . 561  
16-6 Limitations of DSP . . . . . 570  
16-7 DSP Troubleshooting . . . . . 572

Appendix A Solder and the Soldering Process . . . . . 585  
Appendix B Thermionic Devices . . . . . 592  
Appendix C Renewable Energy Sources and Technologies . . . . . 594

[www.mhhe.com/schuler10e](http://www.mhhe.com/schuler10e).

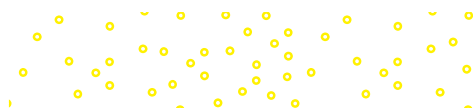Glossary of Terms and Symbols . . . . . 596  
Index . . . . . 608



# Preface

*Electronics: Principles and Applications*, 10e, introduces analog devices, circuits, and systems. It also presents various digital techniques that are now commonly used in what was once considered the sole domain of analog electronics. It is intended for students who have a basic understanding of Ohm's law; Kirchhoff's laws; power; schematic diagrams; and basic components such as resistors, capacitors, and inductors. The digital material is self-contained and will not pose a problem for those students who have not completed a course in digital electronics. The only mathematics prerequisite is a command of basic algebra.

The major objective of this text is to provide entry-level knowledge and skills for a wide range of occupations in electricity and electronics. Its purpose is to assist in the education and preparation of technicians who can effectively diagnose, repair, verify, install, and upgrade electronic circuits and systems. It also provides a solid and practical foundation in analog electronic concepts, device theory, and modern digital solutions for those who may need or want to go on to more advanced study.

The tenth edition, like the earlier ones, combines theory and applications in a logical, evenly paced sequence. It is important that a student's first exposure to electronic devices and circuits be based on a smooth integration of theory and practice. This approach helps the student develop an understanding of how devices such as diodes, transistors, and integrated circuits function and how they are used in practice. Then the understanding of these functions can be applied to the solution of practical problems such as performance analysis and troubleshooting.

This is an extremely practical text. The devices, circuits, and applications are typical of those used in all phases of electronics. Reference is made to common aids such as Internet sites, component identification systems, and substitution guides, and real-world troubleshooting techniques are applied whenever appropriate. The information, theory, and calculations presented are the same as those used by practicing technicians. The formulas presented are immediately applied in examples that make sense and relate to the kinds of calculations actually made by technical workers.

The 16 chapters progress from an introduction to the broad field of electronics through solid-state theory, transistors, and the concepts of gain, amplifiers, oscillators, electronic communications and data transfer, integrated circuits, control circuitry,

regulated power supplies, and digital signal processing. As an example of the practicality of the text, an entire chapter is devoted to troubleshooting circuits and systems. In other chapters, entire sections are devoted to this vital topic. Since the last edition, the electronics industry has continued its march toward more digital and mixed-signal applications to replace what used to be purely analog functions. The distinction between analog and digital continues to blur. This is the only text of its kind that addresses this issue.

## New to this Edition

This edition introduces significant new material in the areas of software updates, integrated circuit communication protocols and power factor correction. Software updates are becoming more of an issue as devices rely more on computers and micro-controllers. It is possible for an update to go awry and render a device inoperable. Mixed signal circuitry is expanded in this edition. The division between the analog and digital worlds has become blurred into non-existence. Chip to chip communication protocols have been added for a better understanding of modern circuitry. Finally, power factor correction has been added. This technology is now becoming commonplace as manufacturers come into compliance with newer standards such as Energy Star Plus put forth by the U.S. Environmental Protection Agency.



This edition is available online with Connect, McGraw Hill Education's integrated assignment and assessment platform. Connect also offers SmartBook for the new edition, which is the first adaptive reading experience proven to improve grades and help students study more effectively. All of the title's website and ancillary content is also available through Connect, including extra review questions, links to industry sites, chapter study overviews, assignments, the Instructor's Manual, and a Multi-Sim Primer, all for students. The following is a list of features that can be found through Connect.

## Instructor Resources

MultiSim Primer (by Patrick Hoppe of Gateway Technical College), which provides a tutorial for new users of the software

Instructor's Manual

PowerPoint presentations for classroom use

Electronic test bank questions for each chapter

Parts and equipment lists

Learning Outcomes

Answers to textbook questions:

Chapter review questions

Critical thinking questions

Answers and data for lab experiments and assignments

Projects

Instrumentation lab experiments in .pdf format

Soldering (.pdf file)

Circuit simulation files (EWB 5 and MultiSim versions 6, 7, 8, 11, and 14)

### Experiments Manual

A correlated Experiments Manual provides a wide array of hands-on labwork, problems, and circuit simulations. MultiSim files are provided for both the simulation activities and the hands-on activities. These files are located on the Student Side of the resources in Connect.

# About the Author

Charles A. Schuler received his Ed.D. from Texas A&M University in 1966, where he was an N.D.E.A. fellow. He has published many articles and seven textbooks on electricity and electronics, almost as many laboratory manuals, and another book that deals with ISO 9000. He taught electronics

technology and electrical engineering technology at California University of Pennsylvania for 30 years. He is currently a full-time writer, as he continues his passion to make the difficult easy to understand.






# Instructors

## Student Success Starts with You

### Tools to enhance your unique voice

Want to build your own course? No problem. Prefer to use an OLC-aligned, prebuilt course? Easy. Want to make changes throughout the semester? Sure. And you'll save time with Connect's auto-grading, too.

**65%**  
Less Time  
Grading

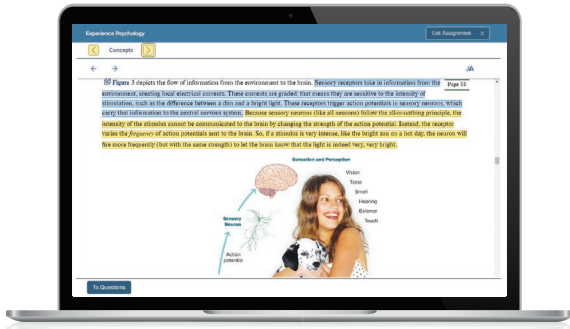

Laptop: Getty Images; Woman/dog: George Doyle/Getty Images

### A unique path for each student

In Connect, instructors can assign an adaptive reading experience with SmartBook<sup>®</sup> 2.0. Rooted in advanced learning science principles, SmartBook 2.0 delivers each student a personalized experience, focusing students on their learning gaps, ensuring that the time they spend studying is time well-spent.

[mheducation.com/highered/connect/smartbook](http://mheducation.com/highered/connect/smartbook)

### Affordable solutions, added value

Make technology work for you with LMS integration for single sign-on access, mobile access to the digital textbook, and reports to quickly show you how each of your students is doing. And with our Inclusive Access program, you can provide all these tools at the lowest available market price to your students. Ask your McGraw Hill representative for more information.

### Solutions for your challenges

A product isn't a solution. Real solutions are affordable, reliable, and come with training and ongoing support when you need it and how you want it. Visit [supportateverystep.com](http://supportateverystep.com) for videos and resources both you and your students can use throughout the term.

## Students


### Get Learning that Fits You

#### Effective tools for efficient studying

Connect is designed to help you be more productive with simple, flexible, intuitive tools that maximize your study time and meet your individual learning needs. Get learning that works for you with Connect.
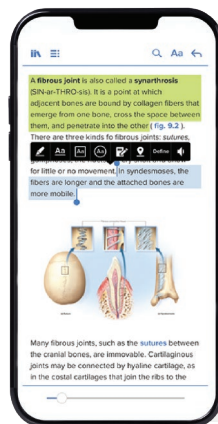
#### Study anytime, anywhere

Download the free ReadAnywhere® app and access your online eBook, SmartBook® 2.0, or Adaptive Learning Assignments when it's convenient, even if you're offline. And since the app automatically syncs with your Connect account, all of your work is available every time you open it. Find out more at [mheducation.com/readanywhere](http://mheducation.com/readanywhere)



*"I really liked this app—it made it easy to study when you don't have your textbook in front of you."*

- Jordan Cunningham,  
Eastern Washington University

iPhone: Getty Images



#### Everything you need in one place

Your Connect course has everything you need—whether reading your digital eBook or completing assignments for class, Connect makes it easy to get your work done.

#### Learning for everyone

McGraw Hill works directly with Accessibility Services Departments and faculty to meet the learning needs of all students. Please contact your Accessibility Services Office and ask them to email [accessibility@mheducation.com](mailto:accessibility@mheducation.com), or visit [mheducation.com/about/accessibility](http://mheducation.com/about/accessibility) for more information.



# Walkthrough

*Electronics: Principles and Applications* takes a concise and practical approach to this fascinating subject. The textbook's easy-to-read style, color illustrations, and basic math level make it ideal for students who want to learn the essentials of modern electronics and apply them to real job-related situations.

## Learning Outcomes

This chapter will help you to:

- 1-1** Identify some major events in the history of electronics. [1-1]
- 1-2** Classify circuit operation as digital or analog. [1-2]
- 1-3** Name major analog circuit functions. [1-3]
- 1-4** Begin developing a system viewpoint for troubleshooting. [1-3]
- 1-5** Analyze circuits with both dc and ac sources. [1-4]
- 1-6** List the current trends in electronics. [1-5]

Each chapter starts with **Learning Outcomes** that give the reader an idea of what to expect in the following pages, and what he or she should be able to accomplish by the end of the chapter. These outcomes are distinctly linked to the chapter subsections.

**Key Terms**, noted in the margins, call the reader's attention to key concepts.

## I-2 Digital or Analog

Today, electronics is such a huge field that it is often necessary to divide it into smaller subfields. You will hear terms such as medical electronics, instrumentation electronics, automotive electronics, avionics, consumer electronics, industrial electronics, and others. One way that electronics can be divided is into digital or analog.

A *digital electronic device* or circuit will recognize or produce an output of only several limited states. For example, most digital circuits will respond to only two input conditions: low or high. *Digital circuits* may also be called *binary* since they are based on a number system with only two digits: 0 and 1.

An *analog circuit* can respond to or produce an output for an infinite number of states. An analog input or output might vary between 0 and 10 volts (V). Its actual value could be 1.5 V, 2.8, or even 9.9 V. In the infinite p...

Digital electronic device

Digital circuit

Analog circuit

Linear circuit

### EXAMPLE 1-1

An audio compact disk (CD) uses 16 bits to represent each sample of the signal. How many steps or volume levels are possible? Use the appropriate power of 2:

$$2^{16} = 65,536$$

This is easy to solve using a calculator with an  $x^y$  key. Press 2, then  $x^y$ , and then 16 followed by the = key.

Numerous solved *Example* problems throughout the chapters demonstrate the use of formulas and the methods used to analyze electronic circuits.

### HISTORY OF ELECTRONICS

#### Niels Bohr and the Atom

Scientists change the future by improving on the ideas of others. Niels Bohr proposed a model of atomic structure in 1913 that applied energy levels (quantum mechanics) to the Rutherford model of the atom. Bohr also used some of the work of Max Planck.



Everett Collection Historical/Alamy Stock Photo

#### You May Recall

Chokes are so named because they “choke off” high-frequency current flow.

*History of Electronics*, *You May Recall*, and *About Electronics* add historical depth to the topics and highlight new and interesting technologies or facts.

### ABOUT ELECTRONICS

#### Materials Used for Dopants, Semiconductors, and Microwave Devices

- Gallium arsenide (GaAs) works better than silicon in microwave devices because it allows faster movement of electrons.
- Materials other than boron and arsenic are used as dopants.
- It is theoretically possible to make semiconductor devices from crystalline carbon.
- Crystal radio receivers were an early application of semiconductors.

All critical facts and principles are reviewed in the *Summary and Review* section at the end of each chapter.

## Chapter 1 Summary and Review

### Summary

1. Electronics is a relatively young field. Its history began in the 20th century.
2. Electronic circuits can be classified as digital or analog.
3. The number of states or voltage levels is limited in a digital circuit (usually to two).
4. An analog circuit has an infinite number of voltage levels.
5. In a linear circuit, the output signal is a replica of the input.
6. All linear circuits are analog, but not all analog circuits are linear. Some analog circuits distort
10. The number of output levels from a D/A converter is equal to 2 raised to the power of the number of bits used.
11. Digital signal processing uses computers to enhance signals.
12. Block diagrams give an overview of electronic system operation.
13. Schematic diagrams show individual part wiring and are usually required for component-level troubleshooting.
14. Troubleshooting begins at the system level.
15. Alternating current and direct current signals are

All of the important chapter formulas are summarized at the end of each chapter in *Related Formulas*. *Chapter Review Questions* are found at the end of each chapter; and separate, more challenging *Chapter Review Problems* sections are available in appropriate chapters.

### Related Formulas

Number of levels in a binary system:  $\text{levels} = 2^n$

Inductive reactance:  $X_L = 2\pi fL$

Capacitive reactance:  $X_C = \frac{1}{2\pi fC}$

### Chapter Review Questions

*Determine whether each statement is true or false.*

- 1-1. Most digital circuits can output only two states, high and low. (1-2)
- 1-2. Digital circuit outputs are usually sine waves. (1-2)
- 1-3. The output of a linear circuit is an exact replica of the input. (1-2)
- 1-4. Linear circuits are classified as analog. (1-2)
- 1-5. All analog circuits are linear. (1-2)
- 1-6. The output of a 4-bit D/A converter can produce 128 different voltage levels. (1-2)
- 1-7. An attenuator is an electronic circuit used to make signals stronger. (1-3)
- 1-8. Block diagrams are best for component-level troubleshooting. (1-3)
- 1-9. In Fig. 1-8, if the signal at point 4 is faulty, then the signal at point 3 must also be faulty. (1-3)
- 1-10. Refer to Fig. 1-8. The power supply should be checked first. (1-3)

Finally, each chapter ends with *Critical Thinking Questions* and *Answers to Self-Tests*.



### Answers to Self-Tests

- |      |       |                 |                         |
|------|-------|-----------------|-------------------------|
| 1. T | 7. T  | 13. F           | 19. capacitors          |
| 2. T | 8. F  | 14. F           | 20. bypass              |
| 3. F | 9. T  | 15. T           | 21. coupling (dc block) |
| 4. T | 10. F | 16. F           | 22. F                   |
| 5. F | 11. F | 17. -7.5 V      | 23. T                   |
| 6. T | 12. T | 18. 12.5 V, 0 V | 24. F                   |

### Critical Thinking Questions

- |  |  |
|--|--|
| 1-1. Functions now accomplished by using electronics may be accomplished in different ways in the future. Can you think of any examples? | 1-3. What could go wrong with capacitor $C_2$ in Fig. 1-10, and how would the fault affect the waveform at Node D? |
| 1-2. Can you describe a simple system that uses only two wires but will selectively signal two different people?                         | 1-4. What could go wrong with capacitor $C_2$ in Fig. 1-13, and how would the fault affect the waveform at Node D? |

# Acknowledgments

Where does one begin? This book was started with a research project. It was tested both in industry and education. The testing led to many refinements that produced a truly effective textbook. Many people contributed to that effort . . . both in education and in industry. Their dedication and diligence helped launch what has become a

remarkably long-lasting and practical work. Then, there are all those instructors and students who have given sage and thoughtful advice over the years. And there are those gifted and hardworking folks at McGraw Hill. Finally, there is my family, who indulge my passion and encourage my efforts.

# Safety

Electric and electronic circuits can be dangerous. Safe practices are necessary to prevent electrical shock, fires, explosions, mechanical damage, and injuries resulting from the improper use of tools.

Perhaps the greatest hazard is electrical shock. A current through the human body in excess of 10 milliamperes can paralyze the victim and make it impossible to let go of a “live” conductor or component. Ten milliamperes is a rather small amount of current flow: It is only *ten one-thousandths* of an ampere. An ordinary flashlight can provide more than 100 times that amount of current!

Flashlight cells and batteries are safe to handle because the resistance of human skin is normally high enough to keep the current flow very small. For example, touching an ordinary 1.5-V cell produces a current flow in the microampere range (a microampere is one one-millionth of an ampere). This amount of current is too small to be noticed.

High voltage, on the other hand, can force enough current through the skin to produce a shock. If the current approaches 100 milliamperes or more, the shock can be fatal. Thus, the danger of shock increases with voltage. Those who work with high voltage must be properly trained and equipped.

When human skin is moist or cut, its resistance to the flow of electricity can drop drastically. When this happens, even moderate voltages may cause a serious shock. Experienced technicians know this, and they also know that so-called low-voltage equipment may have a high-voltage section or two. In other words, they do not practice two methods of working with circuits: one for high voltage and one for low voltage. They follow safe procedures at all times. A 5-V power supply could have internal circuitry that operates at 400 V! They do not assume protective devices are working. They do not assume a circuit is off even though the switch is in the OFF position. They know the switch could be defective.

Even a low-voltage, high-current-capacity system like an automotive electrical system can be quite dangerous. Short-circuiting such a system with a ring or metal watchband can cause very severe burns—especially when the ring or band welds to the points being shorted.

As your knowledge and experience grow, you will learn many specific safe procedures for dealing with electricity and electronics. In the meantime,

1. Always follow procedures.
2. Use service manuals as often as possible. They often contain specific safety information. Read, and comply with, all appropriate material safety data sheets.
3. Investigate before you act.
4. When in doubt, *do not act*. Ask your instructor or supervisor.

## General Safety Rules for Electricity and Electronics

Safe practices will protect you and your fellow workers. Study the following rules. Discuss them with others, and ask your instructor about any you do not understand.

1. Do not work when you are tired or taking medicine that makes you drowsy.
2. Do not work in poor light.
3. Do not work in damp areas or with wet shoes or clothing.
4. Use approved tools, equipment, and protective devices.
5. Avoid wearing rings, bracelets, and similar metal items when working around exposed electric circuits.
6. Never assume that a circuit is off. Double-check it with an instrument that you are sure is operational.
7. Some situations require a “buddy system” to guarantee that power will not be turned on while a technician is still working on a circuit.
8. Never tamper with or try to override safety devices such as an interlock (a type of switch that automatically removes power when a door is opened or a panel removed).
9. Keep tools and test equipment clean and in good working condition. Replace insulated probes and leads at the first sign of deterioration.
10. Some devices, such as capacitors, can store a *lethal* charge. They may store this charge for long periods





of time. You must be certain these devices are discharged before working around them.

11. Do not remove grounds, and do not use adaptors that defeat the equipment ground.
12. Use only an approved fire extinguisher for electrical and electronic equipment. Water can conduct electricity and may severely damage equipment. Carbon dioxide (CO<sub>2</sub>) or halogenated-type extinguishers are usually preferred. Foam-type extinguishers may also be desired in *some* cases. Commercial fire extinguishers are rated for the type of fires for which they are effective. Use only those rated for the proper working conditions.
13. Follow directions when using solvents and other chemicals. They may be toxic or flammable, or they may damage certain materials such as plastics. Always read and follow the appropriate material safety data sheets.
14. A few materials used in electronic equipment are toxic. Examples include tantalum capacitors and beryllium oxide transistor cases. These devices should not be crushed or abraded, and you should wash your hands thoroughly after handling them. Other materials (such as heat shrink tubing) may produce irritating fumes if overheated. Always read and follow the appropriate material safety data sheets.

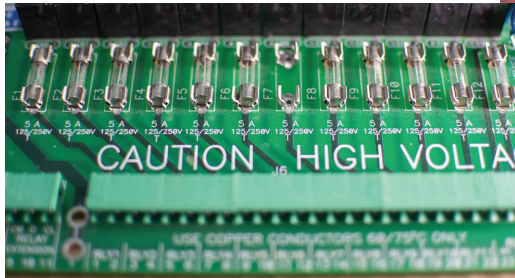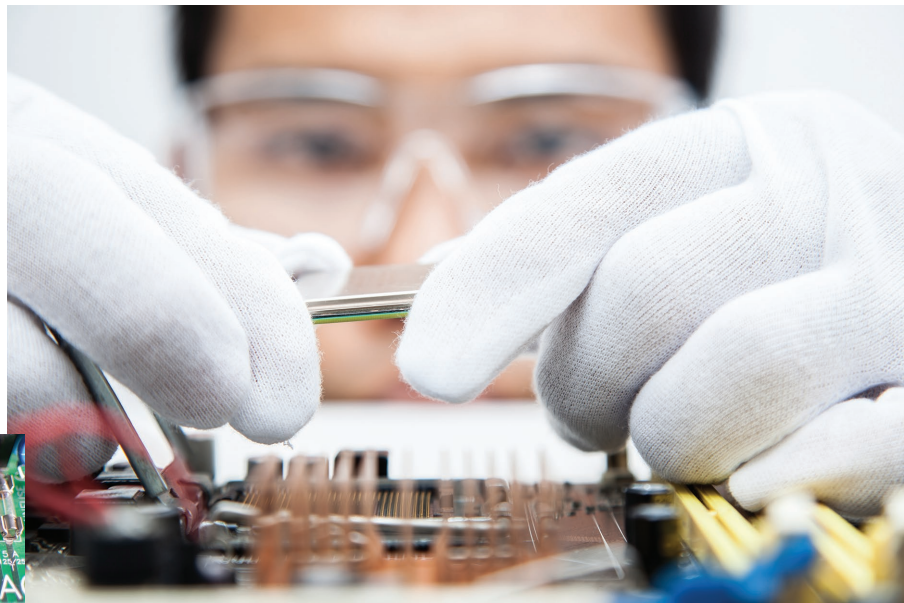15. Certain circuit components affect the safe performance of equipment and systems. Use only exact or approved replacement parts.
16. Use protective clothing and safety glasses when handling high-vacuum devices such as picture tubes and cathode-ray tubes.
17. Don't work on equipment before you know proper procedures and are aware of any potential safety hazards.
18. Many accidents have been caused by people rushing and cutting corners. Take the time required to protect yourself and others. Running, horseplay, and practical jokes are strictly forbidden in shops and laboratories.
19. Never look directly into light-emitting diodes or fiber-optic cables. Some light sources, although invisible, can cause serious eye damage.
20. Lithium batteries can explode and start fires. They must be used only as intended and only with approved chargers. Lead-acid batteries produce hydrogen gas, which can explode. They too must be used and charged properly.

Circuits and equipment must be treated with respect. Learn how they work and the proper way of working on them. Always practice safety: your health and life depend on it.



Electronics workers use specialized safety knowledge.

Yamato1987/iStock/Getty Images; suphakit73/Shutterstock

Design Elements: Answers to Self-Tests (Check Mark): ©McGraw Hill Global Education Holdings, LLC; Horizontal Banner (Futuristic Banner): ©touc/DigitalVision Vectors/Getty Images RF; Internet Connection (Globe): ©Shutterstock/Sarunyu\_foto; Vertical Banner (Hazard Stripes): ©Ingram Publishing

# CHAPTER 1

# Introduction

## Learning Outcomes

This chapter will help you to:

- 1-1** Identify some major events in the history of electronics. [1-1]
- 1-2** Classify circuit operation as digital or analog. [1-2]
- 1-3** Name major analog circuit functions. [1-3]
- 1-4** Begin developing a system viewpoint for troubleshooting. [1-3]
- 1-5** Analyze circuits with both dc and ac sources. [1-4]
- 1-6** List the current trends in electronics. [1-5]

Looking back at electronics in the 20th century shows the inception of major discoveries such as radio, TV, cell phones, computers, medical electronics, and others that changed the path of mankind. The 21st century is seeing even more amazing breakthroughs. There will be ongoing rapid growth and solutions for an imperiled planet. As a career, it is a solid choice. This book was written to help move you along your path. This chapter introduces you to the broad field of electronics and helps you sort things out by building on what you already know about electric circuits and learning how basic electronic functions fit together to make solutions, products, and systems.

## 1-1 A Brief History

It is hard to place an exact date on the beginning of electronics. The year 1899 is one possibility. During that year, J. J. Thomson, at the University of Cambridge in England, discovered the electron. Two important developments at the beginning of the 20th century made people interested in electronics. The first was in 1901, when Guglielmo Marconi sent a message across the Atlantic Ocean using *wireless* telegraphy. Today we call wireless communication *radio*. The second development came in 1906, when Lee De Forest invented the audion vacuum tube. The term *audion* related to its first use, to make sounds (“audio”) louder. It was not long before the wireless inventors used the *vacuum tube* to improve their equipment.

Another development in 1906 is worth mentioning. Greenleaf W. Pickard used the first crystal radio detector. This great improvement helped make radio and electronics more popular. It also suggested the use of *semiconductors* (crystals) as materials with future promise for the new field of radio and electronics.

Audion

Vacuum tube

Semiconductor

Commercial radio was born in Pittsburgh, Pennsylvania, at station KDKA in 1920. This development marked the beginning of a new era, with electronic devices appearing in the average home. By 1937 more than half the homes in the United States had a radio. Commercial television began around 1946. In 1947 several hundred thousand home radio receivers were manufactured and sold. Complex television receivers and complicated electronic devices made technicians wish for something better than vacuum tubes.


The first vacuum tube computer project was funded by the U.S. government, and the research began in 1943. Three years later, the ENIAC was formally dedicated at the Moore School of Electrical Engineering of the University of Pennsylvania on February 15, 1946. It was the world's first electronic digital computer:

- Size: 30 ft × 50 ft
- Weight: 30 tons
- Vacuum tubes: 17,468

- Resistors: 70,000
- Capacitors: 10,000
- Relays: 1,500
- Switches: 6,000
- Power: 150,000 W
- Cost: \$486,000 (about \$8 million today)
- Reliability: 7 minutes mean time between failures (MTBF)

A group of students at the Moore School participated in the fiftieth-year anniversary celebration of the ENIAC by developing an equivalent complementary metal oxide semiconductor (CMOS) chip:

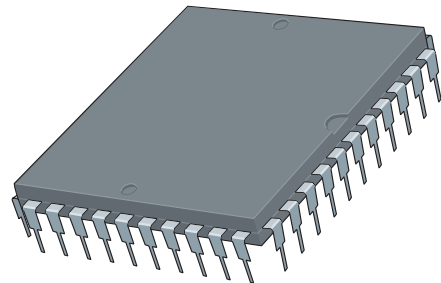- Size: 7.44 mm × 5.29 mm
- Package: 132 pin grid array (PGA)
- Transistors: 174,569
- Cost: several dollars (estimated, per unit, if put into production)
- Power: approximately 1 W
- Reliability: 50 years (estimated)



The vacuum tube, the transistor, and then the integrated circuit. The evolution of electronics can be compared with the evolution of life.

(top left): begemot\_30/123RF

Scientists had known for a long time that many of the jobs done by vacuum tubes could be done more efficiently by semiconducting crystals, but they could not make crystals pure enough to do the job. The breakthrough came in 1947. Three scientists working with Bell Laboratories made the first working transistor. This was such a major contribution to science and technology that the three men—John Bardeen, Walter H. Brattain, and William B. Shockley—were awarded the Nobel Prize.

Around the same time (1948) Claude Shannon, also then at Bell Laboratories, published a paper on communicating in binary code. His work formed the basis for the digital communications revolution, from cell phones to the Internet. Shannon was also the first to apply Boolean algebra to telephone switching networks when he worked at the Massachusetts Institute of Technology in 1940. Shannon's work forms much of the basis for what we now enjoy in both telecommunications and computing.

Improvements in transistors came rapidly, and now they have all but completely replaced the vacuum tube. *Solid state* has become a household term. Many people believe that the transistor is one of the greatest developments ever.

Solid-state circuits were small, efficient, and more reliable. But the scientists and engineers still were not satisfied. Work done by Jack Kilby of Texas Instruments led to the development of the *integrated circuit* in 1958. Robert Noyce, working at Fairchild, developed a similar project. The two men shared a Nobel Prize in Physics for inventing the integrated circuit.

Integrated circuits are complex combinations of several kinds of devices on a common base, called a *substrate*, or in a tiny piece of silicon. They offer low cost, high performance, good efficiency, small size, and better reliability than an equivalent circuit built from separate parts.

The complexity of some integrated circuits allows a single chip of silicon only 0.64 centimeter (cm) [0.25 inch (in.)] square to replace huge pieces of equipment. Although the chip can hold thousands of transistors, it still has diodes, resistors, and capacitors too!

In 1971 Intel Corporation in California announced one of the most sophisticated of all integrated circuits—the microprocessor. A *microprocessor* is most of the circuitry of a computer reduced to a single integrated circuit. Microprocessors, some containing the equivalent of billions of transistors, have provided billions of dollars worth of growth for the electronics industry and have opened up entire new areas of applications.

The Intel 4004 contained 2,300 transistors, and today a Xeon processor has more than 6 billion. The 4004 had features as small as 10 micrometers ( $\mu\text{m}$ ), and today the feature size is shrinking toward 10 nanometers (nm).

In 1977 the cellular telephone system entered its testing phase. Since then, the system has experienced immense growth. Its overwhelming success has fostered the development of new technology, such as digital communications and linear integrated circuits for communications.

In 1982, Texas Instruments offered a single chip digital signal processor (DSP). This made it practical to apply DSP to many new product designs. The growth has continued ever since, and DSP is now one of the most rapidly expanding segments of the semiconductor industry.

The integrated circuit is producing an electronics explosion. Now electronics is being applied in more ways than ever before. At one time radio was almost its only application. Today electronics makes a major contribution to our society and to every field of human endeavor. It affects us in ways we may not be aware of. We are living in the electronic age.

Microprocessor

Solid state

Integrated circuit

Substrate

## Self-Test

Determine whether each statement is true or false.

1. Electronics is a young technology that began in the 20th century.
2. The early histories of radio and electronics are closely linked.
3. Transistors were invented before vacuum tubes.
4. A modern integrated circuit can contain thousands of transistors.
5. A microprocessor is a small circuit used to replace radio receivers.

## I-2 Digital or Analog

Today, electronics is such a huge field that it is often necessary to divide it into smaller subfields. You will hear terms such as medical electronics, instrumentation electronics, automotive electronics, avionics, consumer electronics, industrial electronics, and others. One way that electronics can be divided is into digital or analog.

A *digital electronic device* or circuit will recognize or produce an output of only several limited states. For example, most digital circuits will respond to only two input conditions: low or high. *Digital circuits* may also be called *binary* since they are based on a number system with only two digits: 0 and 1.

An *analog circuit* can respond to or produce an output for an infinite number of states. An analog input or output might vary between 0 and 10 volts (V). Its actual value could be 1.5, 2.8, or even 7.653 V. In theory, an *infinite* number of voltages are possible. On the other hand, one type of digital circuit recognizes inputs ranging from 0 to 0.4 V as low (binary 0) and those ranging from 2.0 to 5 V as high (binary 1). This type of digital circuit does not respond any differently for an input of 2 V than it does for one at 4 V. Both of these voltages are in the high range. Input voltages between 0.4 and 2.0 V are not allowed in digital systems because they cause an output that is unpredictable.

For a long time, almost all electronic devices and circuits operated in the analog fashion. This seemed to be the most obvious way to do a particular job. After all, most of the things that we measure are analog in nature. Your height, weight, and the speed at which you travel in a car are all analog quantities. Your voice is analog. It contains an infinite number of levels and frequencies. So, if you wanted a circuit to amplify your voice, you would probably think of using an analog circuit.

Telephone switching and computer circuits forced engineers to explore digital electronics. They needed circuits and devices to make logical decisions based on certain input conditions. They needed highly reliable circuits that would always operate the same way. By limiting the number of conditions or states in which the circuits must operate, they could be made more reliable. An infinite number of states—the analog circuit—were not what they needed.

Figure 1-1 gives examples of circuit behavior to help you identify digital or analog operation. The signal going into the circuit is on the left, and the signal coming out is on the right. For now, think of a signal as some electrical quantity, such as voltage, that changes with time. The circuit marked *A* is an example of a digital device. Digital waveforms are rectangular. The output signal is a rectangular wave; the input signal is not exactly a rectangular wave. Rectangular waves have only two voltage levels and are very common in digital devices.

Circuit *B* in Fig. 1-1 is an analog device. The input and the output are sine waves. The output is larger than the input, and it has been shifted above the zero axis. The most important feature is that the output signal is a combination of an infinite number of voltages. In a *linear circuit*, the output is an exact replica of the input. Though circuit *B* is linear, not all analog circuits are linear. For example, a certain audio amplifier could have a distorted sound. This amplifier would still be in the analog category, but it would be nonlinear.

Circuits *C* through *F* are all digital. Note that the outputs are all *rectangular* waves (two levels of voltage). Circuit *F* deserves special attention. Its input is a rectangular wave. This could be an analog circuit responding to only two voltage levels except that something has happened to the signal, which did not occur in any of the other examples. The output frequency is different from the input frequency. Digital circuits that accomplish this are called *counters*, or *dividers*.

It is now common to convert analog signals to a digital format that can be stored in computer memory, on magnetic or optical disks, or on magnetic tape. Digital storage has advantages. Everyone who has heard music played from a digital disk knows that it is usually noise free. Digital recordings do not deteriorate with use as analog recordings do.

Another advantage of converting analog signals to digital is that computers can then be used to enhance the signals. Computers are digital machines. They are powerful, high-speed number crunchers. A computer can do various things to signals such as eliminate noise and distortion, correct for frequency and phase errors, and identify signal patterns. This area of electronics is known as digital signal

Digital  
electronic  
device

Digital circuit

Analog circuit

Linear circuit

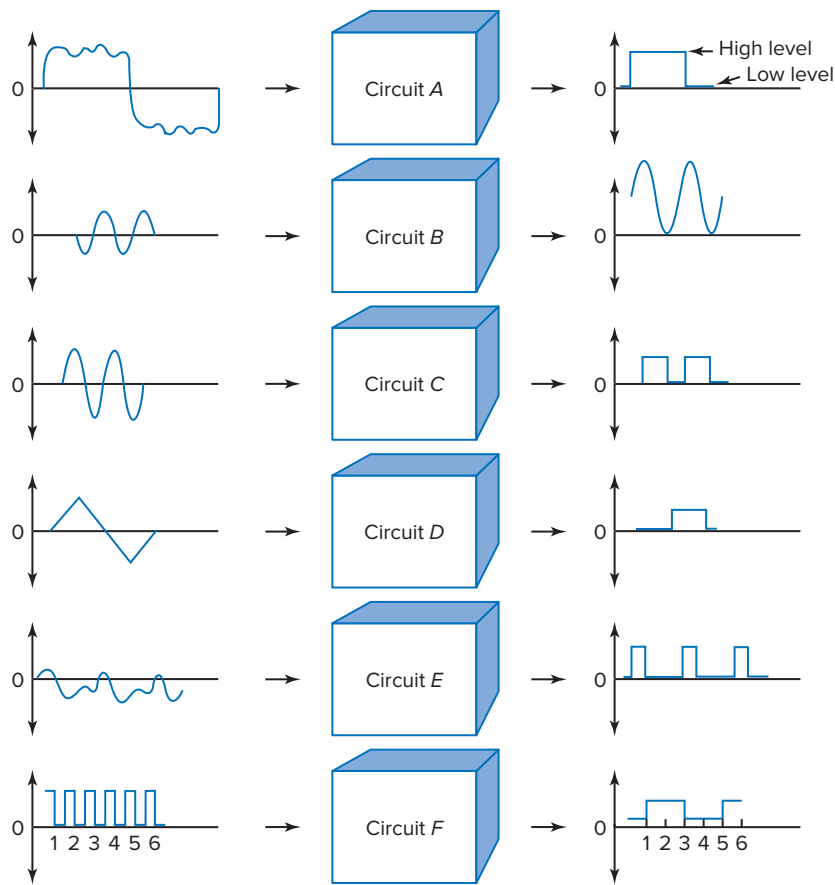


Fig. 1-1 A comparison of digital and analog circuits.

processing (DSP). DSP is used in medical electronics to enhance scanned images of the human body, in audio to remove noise from old recordings, and in many other ways. DSP is covered in Chap. 16.

Figure 1-2 shows a system that converts an analog signal to digital and then back to analog. An *analog-to-digital (A/D) converter* is a circuit that produces a binary (only 0s and 1s) output. Note that the numbers stored in memory are

**A/D converter**

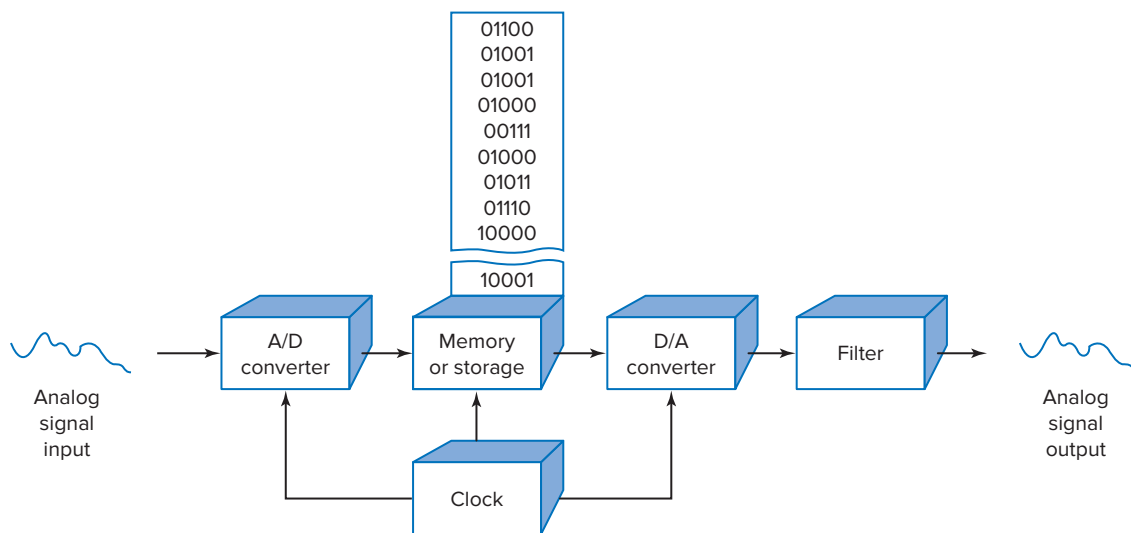


Fig. 1-2 An analog-to-digital-to-analog system.

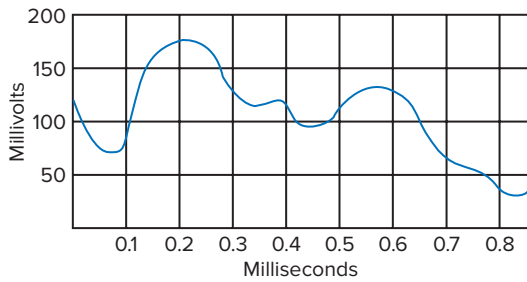


Fig. 1-3 An analog waveform.

binary. A clock (a timing circuit) drives the A/D converter to sample the analog signal on a repetitive basis. Figure 1-3 shows the analog waveform in greater detail. This waveform is sampled by the A/D converter every 20 microseconds ( $\mu\text{s}$ ). Thus, over a period of 0.8 millisecond (ms), forty samples are taken. The required sampling rate for any analog signal is a function of the frequency of that signal. The higher the frequency of the signal, the higher the sampling rate.

Refer back to Fig. 1-2. The analog signal can be recreated by sending the binary contents of memory to a *digital-to-analog (D/A) converter*. The binary information is clocked out of memory at the same rate as the original signal was sampled. Figure 1-4(a) shows the output of the D/A converter. It can be seen that the waveform is not exactly the same as the original analog signal. It is a series of discrete steps. However, by using more steps, a much closer representation of the original signal can be achieved, as shown in Fig. 1-4(b). Step size is determined by the number of binary digits (bits) used. The number of steps is found by raising 2 to the power of the number of bits. A 5-bit system provides

$$2^5 = 32 \text{ steps}$$

An 8-bit system would provide

$$2^8 = 256 \text{ steps}$$

#### EXAMPLE 1-1

An audio compact disk (CD) uses 16 bits to represent each sample of the signal. How many steps or volume levels are possible? Use the appropriate power of 2:

$$2^{16} = 65,536$$

This is easy to solve using a calculator with an  $x^y$  key. Press 2, then  $x^y$ , and then 16 followed by the = key.

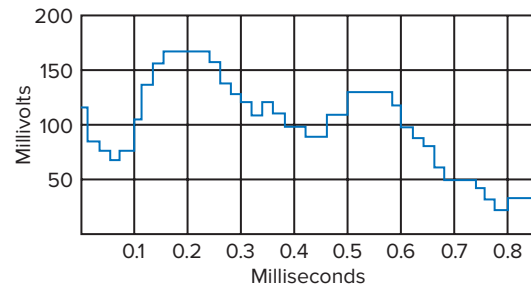


Fig. 1-4(a) Output of the D/A converter.

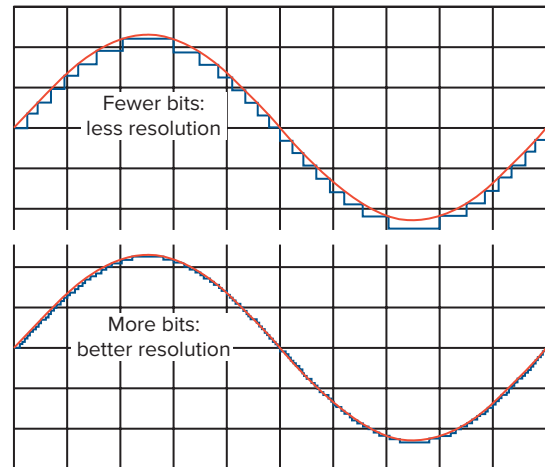


Fig. 1-4(b) More bits gives a better signal representation.

Actually, the filter shown in Fig. 1-2 smooths the steps, and the resulting analog output signal would be quite acceptable for many applications such as speech.

If enough bits and an adequate sampling rate are used, an analog signal can be converted into an accurate digital equivalent. The signal can be converted back into analog form and may not be distinguishable from the original signal. Or it may be noticeably better if DSP is used.

Analog electronics involves techniques and concepts different from those of digital electronics. The rest of this book is devoted mainly to analog electronics. Today most electronic technicians must have skills in both analog and digital circuits and systems.

The term *mixed signal* refers to applications or devices that use both analog and digital techniques. Mixed-signal integrated circuits are covered in Chap. 13.

## Self-Test

Determine whether each statement is true or false.

- Electronic circuits can be divided into two categories, digital or analog.
- An analog circuit can produce an infinite number of output conditions.
- An analog circuit recognizes only two possible input conditions.
- Rectangular waves are common in digital systems.
- D/A converters are used to convert analog signals to their digital equivalents.
- The output of a 2-bit D/A converter can produce eight different voltage levels.

### I-3 Analog Functions

This section presents an overview of some functions that analog electronic circuits can provide. Complex electronic systems can be broken down into a collection of individual functions. An ability to recognize individual functions, how they interact, and how each contributes to system operation will make system analysis and troubleshooting easier.

Analog circuits perform certain operations. These operations are usually performed on *signals*. Signals are electrical quantities, such as voltages or currents, that have some merit or use. For example, a microphone converts a human voice into a small voltage whose frequency and level change with time. This small voltage is called an *audio signal*.

Analog electronic circuits are often named after the function or operation they provide. *Amplification* is the process of making a signal larger or stronger, and circuits that do this are called *amplifiers*. Here is a list of the major types of analog electronic circuits.

- Adders*: Circuits that add signals together. *Subtractors*, also called *difference amplifiers*, are also available.
- Amplifiers*: Circuits that increase signal voltage, current, or power.
- Attenuators*: Circuits that decrease signal levels.
- Clippers*: Devices that prevent signals from exceeding a fixed amplitude limit or limits.
- Comparators*: Devices that compare signal voltage to a reference voltage. Some have one threshold voltage, and others have two.
- Controllers*: Devices that regulate signals and load devices. For example, a controller might be used to set and hold the speed of a motor.
- Converters*: Devices that change a signal from one form to another (e.g., voltage-to-frequency and frequency-to-voltage converters).
- Differentiators*: Circuits that respond to rapidly changing events. They may also be called *high-pass filters*.
- Demultiplexer*: A device that routes one circuit or device into many or one output path into several.
- Detectors*: Devices that remove or recover information from a signal (a radio detector removes voice or music from a radio signal). They are also called *demodulators*.
- Dividers*: Devices that arithmetically divide a signal.
- Filters*: Devices that remove unwanted frequencies from a signal by allowing only those that are desired to pass through.
- Integrator*: A circuit that sums over some time interval.
- Inverters*: Devices that convert direct current (dc) to alternating current (ac).
- Mixers*: Another name for adders; also, nonlinear circuits that produce the sum and difference frequencies of two input signals.
- Modulators*: Devices that allow one signal to control another's amplitude, frequency, or phase.
- Multiplexer*: A device that routes many circuits or devices into one; several signal

## Signals



## Troubleshooting

- sources are combined or selected for one output.
18. *Multipliers*: Devices that perform arithmetic multiplication of some signal characteristic. There are frequency and amplitude multipliers.
  19. *Oscillators*: Devices that convert dc to ac.
  20. *Rectifiers*: Devices that change ac to dc.
  21. *Regulators*: Circuits that hold some value, such as voltage or current, constant.
  22. *Sensors*: Circuits that convert some physical characteristic into a voltage or current.
  23. *Source*: The origin of a type of energy—voltage, current, or power.
  24. *Switches*: Devices that turn signals on or off or change the signal path in an electronic system.
  25. *Timers*: Devices that control or measure time.
  26. *Trigger*: A circuit that activates at some circuit value and usually produces an output pulse.

## Schematic diagram

A *schematic diagram* shows all the individual parts of a circuit and how they are interconnected. Schematics use standard symbols to represent circuit components.

## Block diagram

A *block diagram* shows all the individual functions of a system and how the signals flow through the system. Schematic diagrams are usually required for what is known as

*component-level troubleshooting*. A component is a single part, such as a resistor, capacitor, or an integrated circuit. Component-level repair requires the technician to isolate and replace individual parts that are defective.

System-level repair often requires only a block diagram or a knowledge of the block diagram. The technician observes symptoms and makes measurements to determine which function or functions are improper. Then an entire module, panel, or circuit board is replaced. Component-level troubleshooting usually takes longer than system-level does. Since time is money, it may be economical to replace entire modules or circuit boards.

*Troubleshooting* begins at the system level. Using a knowledge of circuit functions and the block diagram, observation of the symptoms, and measurements, the technician isolates the difficulty to one or more circuit functions. If replacement boards or modules are on hand, one or more functions can be replaced. However, if component-level troubleshooting is required, the technician continues the isolation process to the component level, often by using a voltmeter and an oscilloscope.

Figure 1-5 shows one block of a block diagram for you to see the process. Troubleshooting is often a series of simple yes or no decisions. For example, is the output signal shown in Fig. 1-5 normal? If so, there is no need to troubleshoot that circuit function. If it is not normal, four possibilities exist: (1) a power supply problem, (2) an input signal problem, (3) defective block (function), or (4) some combination of these three items. Voltmeters and/or oscilloscopes are generally used to verify the power supply and the input signal to a block. If the supply and input signals are normal, then the block can be replaced or component-level troubleshooting on that circuit function can begin. The following chapters in this book detail how electronic circuits work and cover component-level troubleshooting.



Technician inspecting a circuit board.

John A. Rizzo/Getty Images



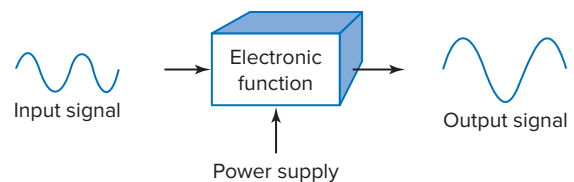



Fig. 1-5 One block of a block diagram.

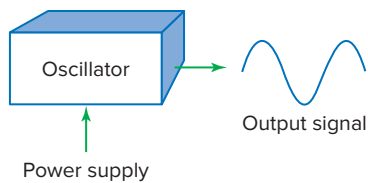

**Fig. I-6** A block with only a power supply input.

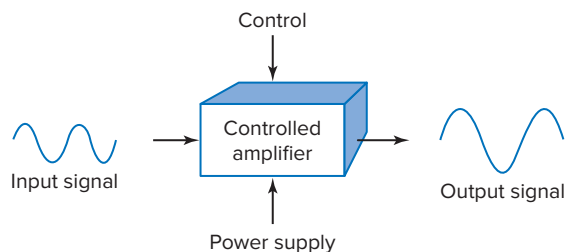

**Fig. I-7** Amplifier with a control input.

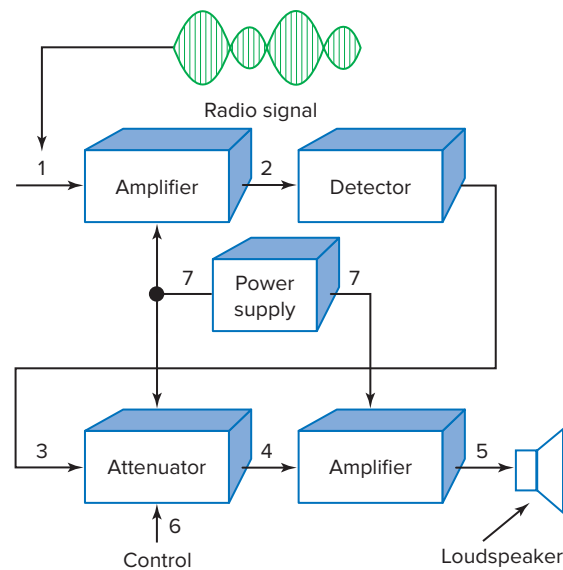

**Fig. I-8** Partial block diagram of a radio receiver.

Figure 1-6 shows a block with only one input (power) and one output. Assuming the output signal is missing or incorrect, the possibilities are: (1) the power supply is defective, (2) the oscillator is defective, or (3) both are defective.

Figure 1-7 shows an amplifier that is controlled by a separate input. If its output signal is not correct, the possible causes are: (1) the power supply is defective, (2) the input signal is defective, (3) the control input is faulty, (4) the amplifier has malfunctioned, or (5) some combination of these four items.

Figure 1-8 illustrates a partial block diagram for a radio receiver. It shows how signals flow through the system. A radio signal is amplified, detected, attenuated, amplified again, and then sent to a loudspeaker to produce sound. Knowing how the signal moves from block to block enables a technician to work efficiently. For

example, if the signal is missing or weak at point 5, the problem could be caused by a bad signal at point 1, or any of the blocks shown might be defective. The power supply should be checked first, since it affects most of the circuit functions shown. If it checks out good, then the signal can be verified at point 1, then point 2, and so on. A defective stage will quickly be located by this orderly process. If the signal is normal at point 3 but not at point 4, then the attenuator block and/or its control input is bad.

Much of this book is devoted to the circuit details needed for component-level troubleshooting. However, you should remember that troubleshooting begins at the system level. Always keep a clear picture in your mind of what the individual circuit function is and how that function can be combined with other functions to accomplish system operation.

## Self-Test

*Determine whether each statement is true or false.*

12. Amplifiers make signals larger.
13. If a signal into an amplifier is normal but the output is not, then the amplifier has to be defective.
14. Component-level troubleshooting requires only a block diagram.
15. A schematic diagram shows how individual parts of a circuit are connected.
16. The first step in troubleshooting is to check individual components for shorts.